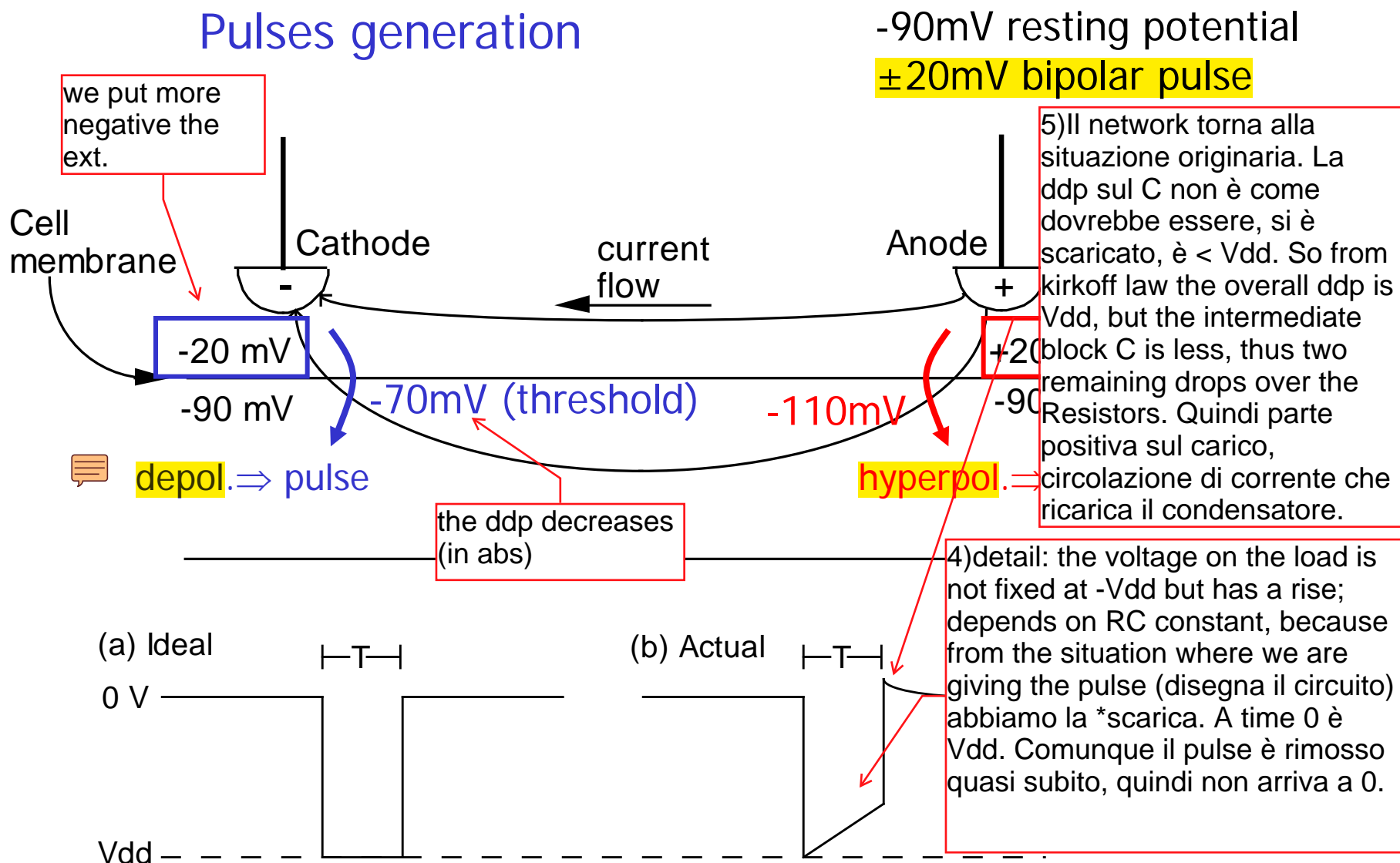


Pulses generation




1) Problematic: the two points are connected :(. With unipolar one el. is simply far away. On the cathode we are supplying -20mv, on the anode +20mV. Stimulating from the external part of the membrane. Where does the AP takes place? On the CATHODE region, we have a resting pot. of -90mV between inside/outside. If we are lowering the voltage outside the membrane by -20mV, the NET effect is to REDUCE THE INTERMEMBRANE POTENTIAL TO -70mV. "less negative". This creates an AP. On the ANODE we hyperpolarize.

UNIPOLAR SYSTEM, we need provide a negative pulse


Pulses generator (basic)

common emitter

(a) Circuit

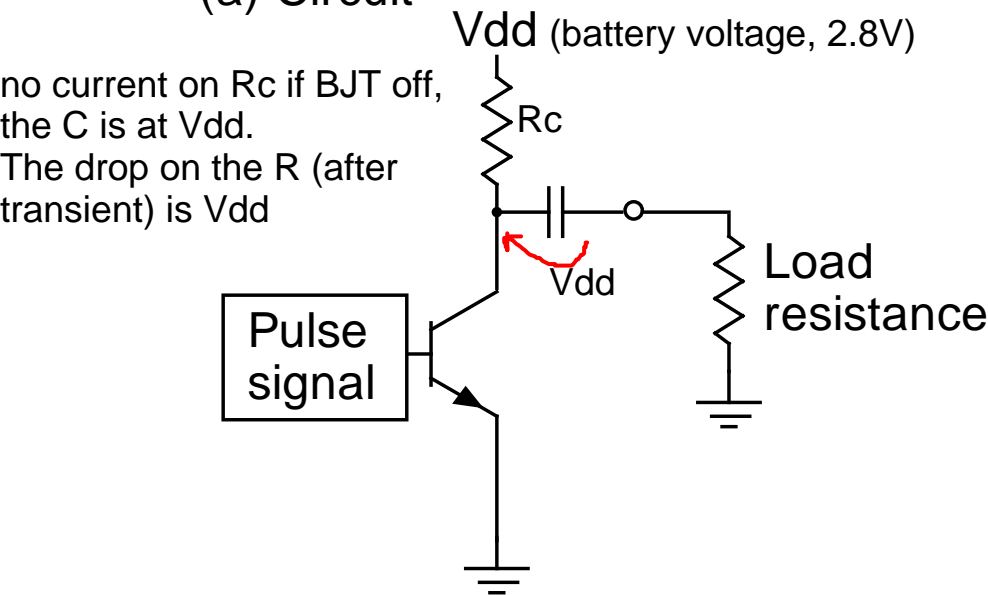


(b) Output

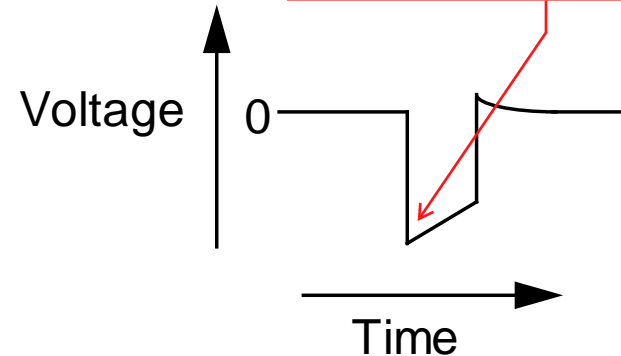

in realtà $-V_{dd}$ is not sufficient :
(see slide 6, overlooked detail.
We need more.

2)(descrizione fatta per il MOS) Then we supply a voltage, we switch on the transistor, and thus the drain drops down because there's a current across the R. V_{ds} at limits goes to 0. Thus over the cap we go from v_{dd} to 0 (node C). The cap is storing charge, if that extremity goes to zero, the other goes to $-V_{dd}$. Thus we provide negative voltage to the load. TRICK: have a precharged capacitor of V_{dd} ! After 1mS you stop the pulse.


Generation of $V > V_{\text{supply}}$

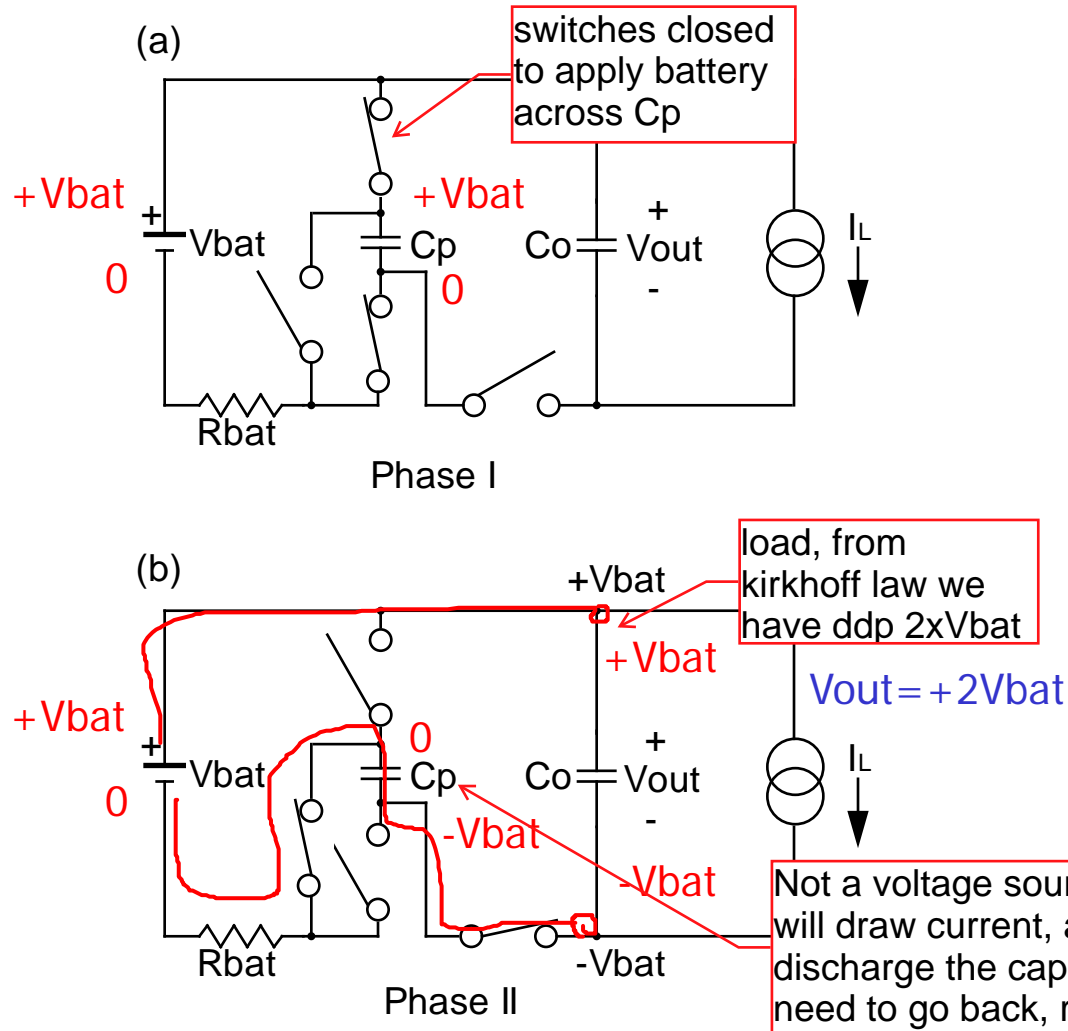

We need to provide more than V_{dd} , at least twice, due to the voltage partition. We precharge a cap with V_{battery} , and then we use it in series with the battery.

same thing, a bit more complex


Pulses generator (unipolar)

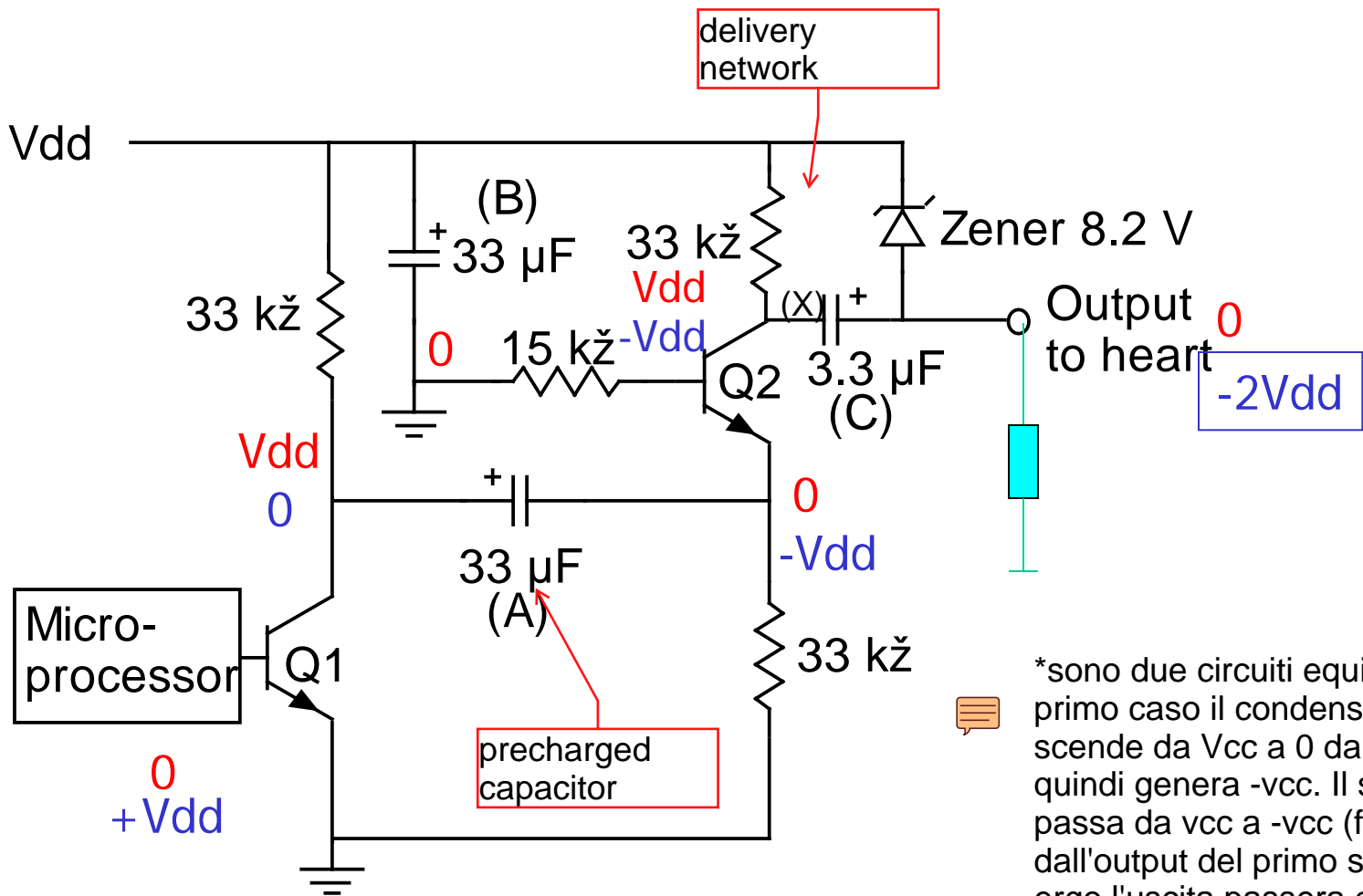


*sono due circuiti equivalenti, nel primo caso il condensatore scende da Vcc a 0 da un lato, quindi genera -vcc. Il secondo passa da vcc a -vcc (fornito dall'output del primo stadio). ergo l'uscita passera da 0 a -2vcc.

"the charges are not changed immediately and thus the right part goes to -Vdd"


Pulses generator (bipolar)

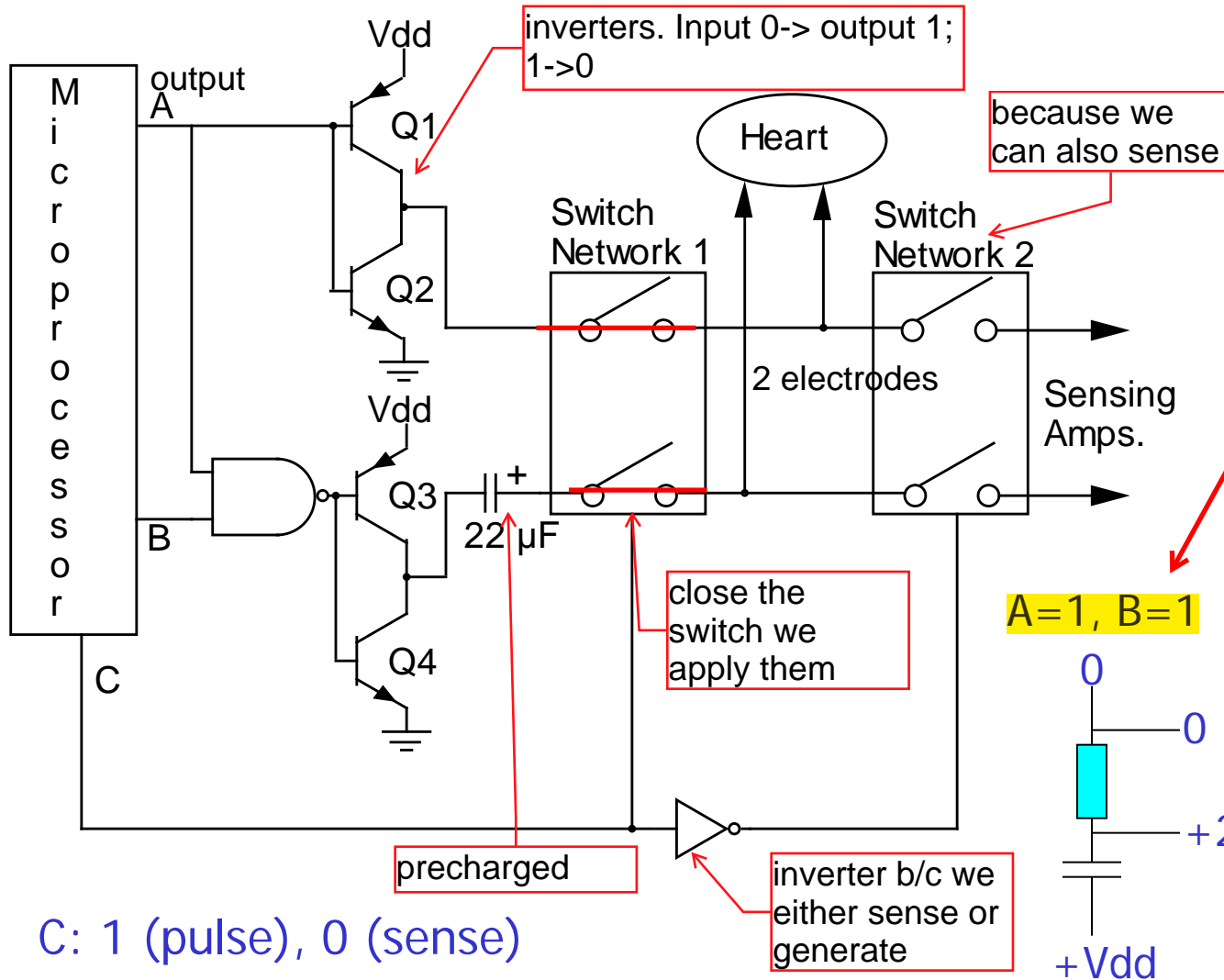

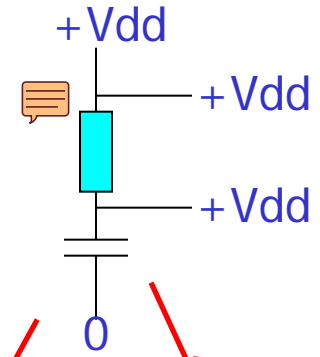
3 situations of the network
 $A=0, B=0$
 (charge of 22 μ f)



$A=1, B=0$

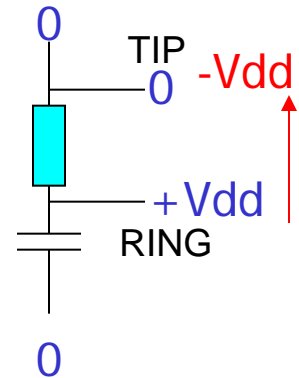


$A=1, B=1$

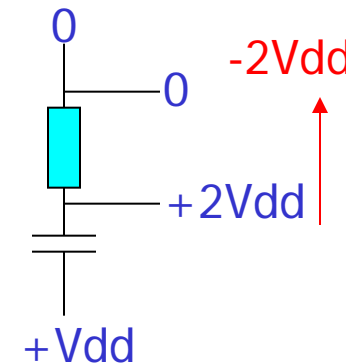

C: 1 (pulse), 0 (sense)


Current vs. pulse duration

We first observe that:

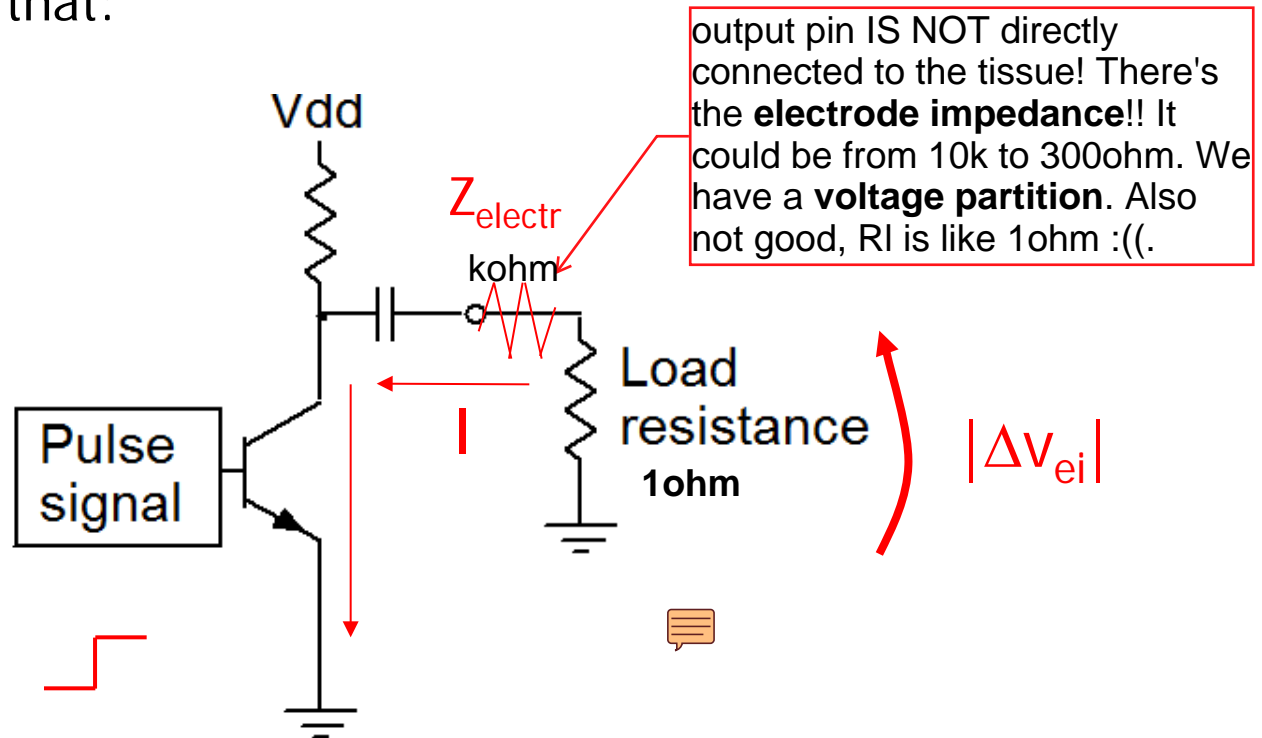

- 1) Due to $Z_{\text{electr}} \gg R_{\text{load}}$, $\Rightarrow |\Delta V_{ei}| \ll V_{dd}$ (that's why we tried to increase Vdd)
- 2) $I \sim V_{dd}/Z_{\text{electr}}$ (it does not depend on the load and it is increased by means of Vdd)

Current vs. pulse duration

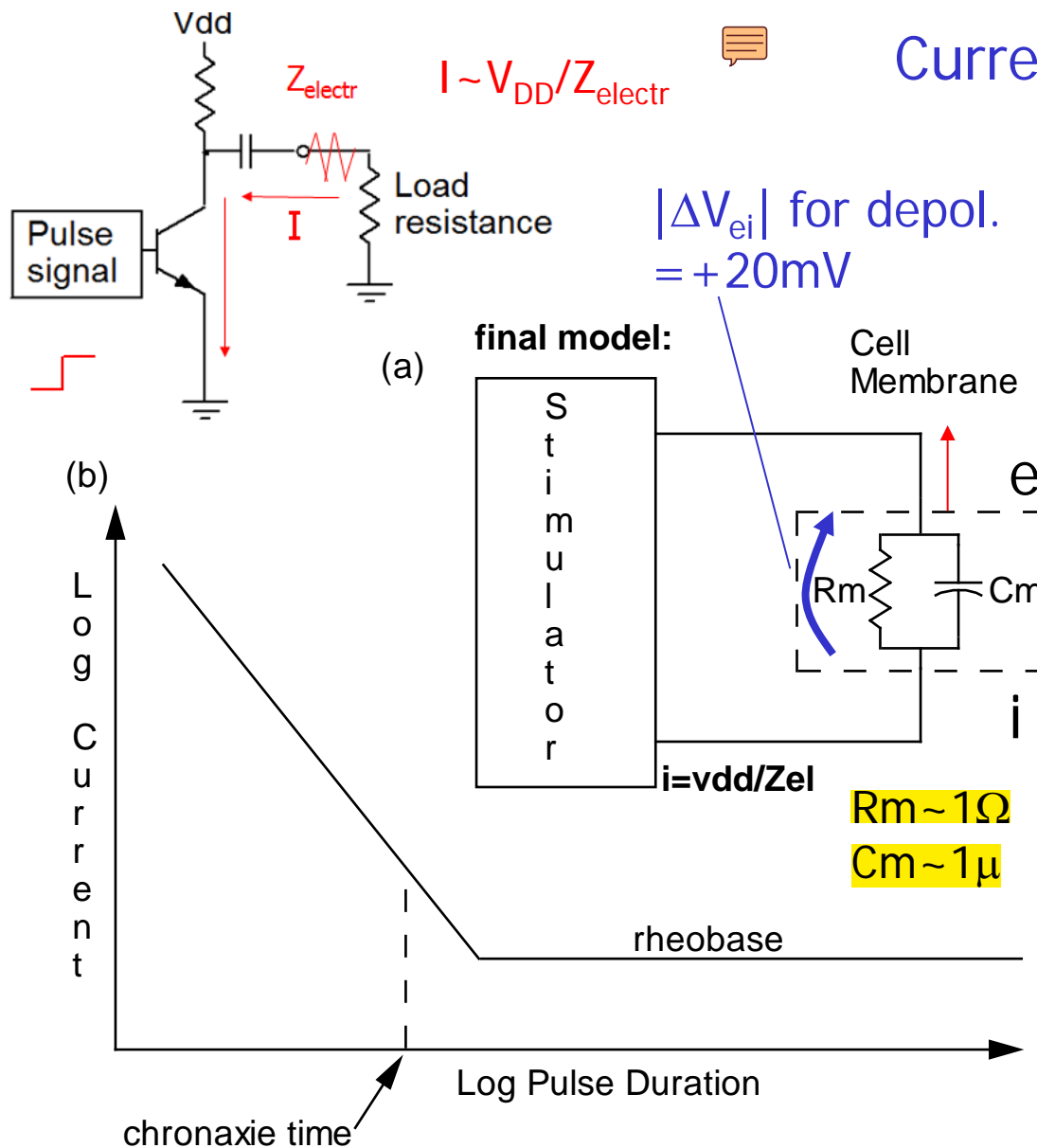


- We need a large V_{DD} to create the minimum ΔV of 20mV on the load
- The load can be represented by a C_m in parallel to a R_m
- If we think in terms of current I (instead of V_{DD}), we can determine a minimum current I necessary to provide 20mV of stimulation:

$$V = IR(1 - e^{-t/RC})$$

$$I = 20 \text{ mV} / 1 \Omega = 20 \text{ mA}$$

*cioè, $V_{del}/Z_{el} \Rightarrow 20\text{mA}$

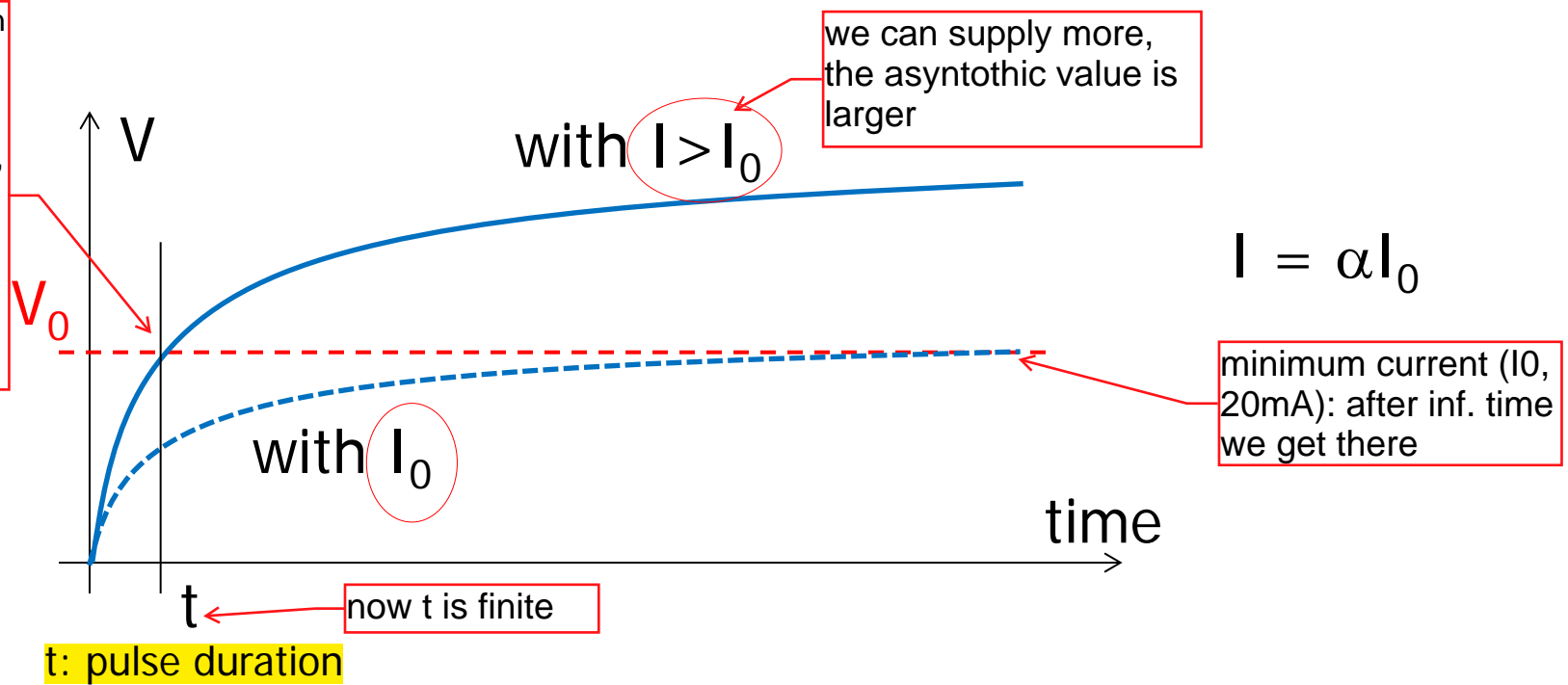we still stop when we reach 20mV. Potrei anche fare supply di current ancora maggiore, ma per tempo minore (impulso maggiore, più stretto). Ho bisogno di più Vdd



$$V_0 = \alpha I_0 R (1 - e^{-t/RC})$$

alpha: multiplying factor >1 , how much larger than I_0 should I supply

V_0 can be reached
with $I = I_0$ ($\alpha = 1$), but with a pulse duration $t \rightarrow \infty$
or
with $I > I_0$ and a finite pulse duration t

\Rightarrow which is the best compromise for I and t ?

*per realizzare AP devo depolarizzare di 20mV. Considerando l'impedenza $R_m = 1\text{ohm}$, il minimo è 20mA di stimolo per tempo finito. Se fornisco una corrente maggiore allora il tempo per dep. a 20mV si riduce. In questo caso viene considerata anche C_m !

Relationship between current and duration.

$$V_0 = \alpha I_0 R (1 - e^{-t/RC})$$

V_0 is 20mV. t is the time to reach 20mV

$$\frac{V_0}{\alpha I_0 R} = (1 - e^{-t/RC}) \quad -\frac{t}{RC} = \ln(1 - \frac{V_0}{\alpha I_0 R})$$

approx if time is low

$$\ln(1+x) \approx x$$

$$\frac{t}{RC} \approx \frac{V_0}{\alpha I_0 R}$$

$$t \approx \cancel{RC} \frac{V_0}{\alpha I_0 \cancel{R}}$$

inverse
proportionality
between I and t
(for large I)

multiply and divide for I_0 :

$$t = C \frac{V_0}{I} \quad I = C \frac{V_0}{t} \frac{I_0}{I_0} \quad I = I_0 \frac{t_c}{t} \quad (t_c = CV_0/I_0)$$

$I=I_0$

$$I = I_0 \frac{t_c}{t}$$

OK for t small

se il tempo che ci vogliamo mettere è
inf allora deve venire fuori I_0 !



we can add +1 to fix this..:

$$I = I_0 (1 + t_c / t)$$


($I \rightarrow I_0$ for $t \rightarrow \infty$) Now it works

no OK for $t \rightarrow \infty$

(does not go to I_0) I goes to 0 :(

key point: charge consumption for the battery. How much charge is delivered in the two pulses? they are not the same (*il tempo si stringe non linearmente con l'intensità).

$t \Rightarrow$ tempo che vogliamo

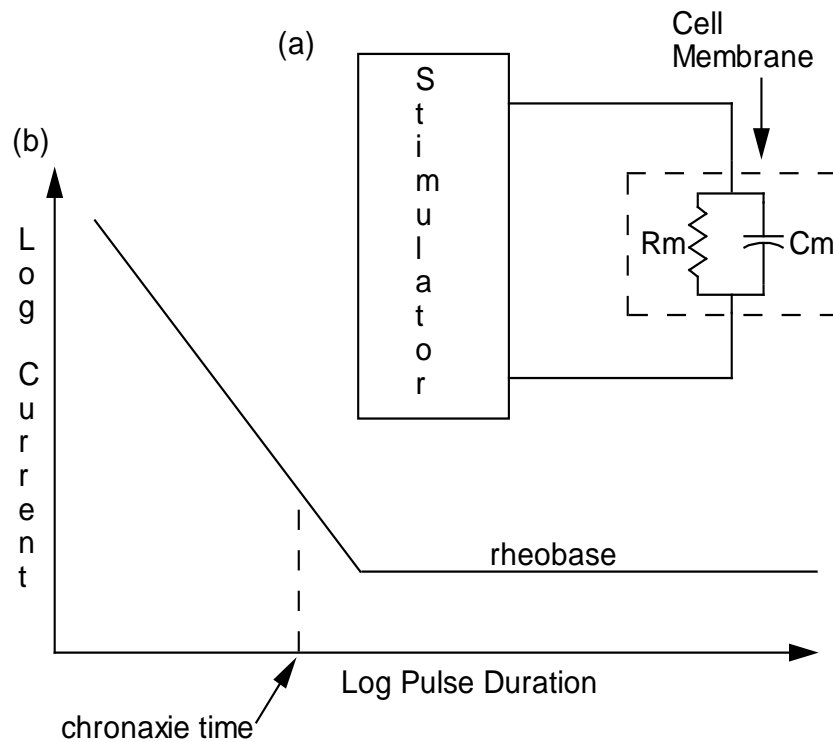

$$\frac{dE}{dt} = 0 \quad \text{for } t = t_c \Rightarrow \boxed{I = 2I_0}$$

$$I = I_0 (1 + t_c / t)$$

which is the best compromise for I and t ?

⇒ minimize the energy consumption (not power)!

$$E = I^2 Z t \quad \text{En=Power*time}$$

we put the I calculated:

$$\frac{dE}{dt} = I_0^2 Z \left(1 - \frac{t_c^2}{t^2}\right)$$

minimization ⇒
we put $d/dt = 0$

$$E = (2I_0)^2 Z t_c = \underline{4I_0^2 Z t_c} \quad \text{best case}$$

$$E = \underline{7.2I_0^2 Z t_c} \quad (t = 0.2t_c) \quad \text{small } t$$

$$E = \underline{4.5I_0^2 Z t_c} \quad (t = 2t_c)$$

We consider constant impedance. We put the current calculated, we obtain that the CURRENT IS TWICE THE I_0 . Optimum current for minimum energy consumption: is in between, not too high, not the minimum. **We set 40mA.**