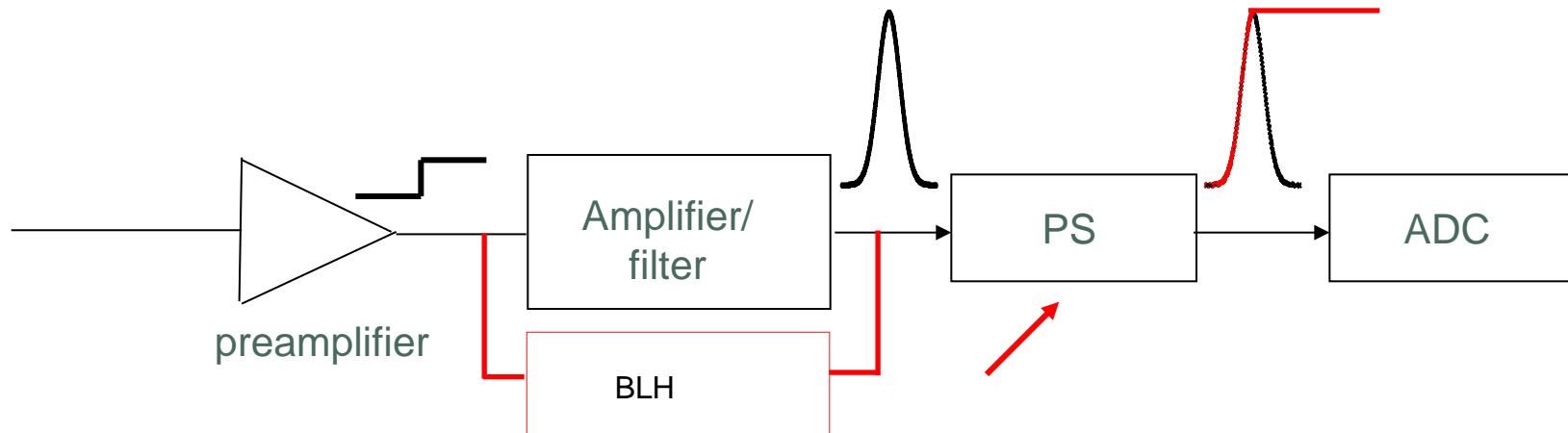


The Peak Stretcher




goal: to stretch the signal peak at the filter output for the time **necessary for the ADC conversion**

Peak stretch: "stretch" the peak of gaussian pulse, b/c amplitude of gaussian is the information we need, but it last for few time. So in this way the adc can convert in time. Once the conversion is done => reset.

The traditional Peak Stretcher

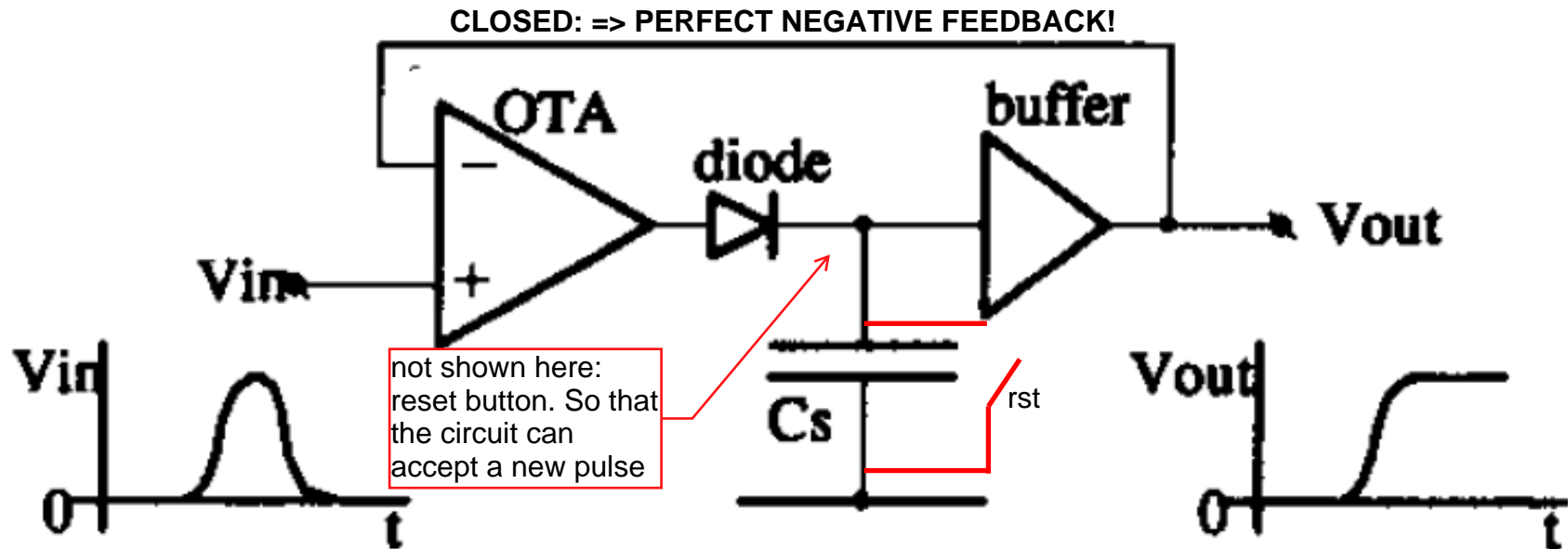
problem: Diode not implemented in CMOS :(We want the same circuit but with a substitute for it




OTA = operational amplifier but with current output. buffer to separate cap. from world. Then loop closed.

EXPL: V_{in} like the drawing, $C_s = 0V$ at the beginning, the buffer keeps the "-" at $0V$. When V_{in} starts to grow, $V_+ > V_-$, the OTA starts providing a positive output, drives the diode (sends current). With this polarity the diode turns on and charges the cap. **THE LOOP IS CLOSED IF THE DIODE IS TURNED ON => perfect negative feedback.** the buffer transfers V_{cs} , so also V_- starts to grow up. Since there's a loop a virtual short circuit is established between the two inputs. Thus, if we have a short circuit V_- and V_+ the output is following V_+ , thus we have a buffer, enabled by the Diode ON. When the input starts to decrease (After the peak), V_+ starts to drop, the negative input is still high. So we have an inversion of polarity at the input of OTA, thus the output starts to get negative (current in the other direction) but this is not possible, due to the diode, which turns off, and the loop is open. [2 phases: 1 loop closed it works as a buffer, 2 loop open, C_s stops to be charged, the C_s holds the final value of the peak voltage, and the output is kept at this]

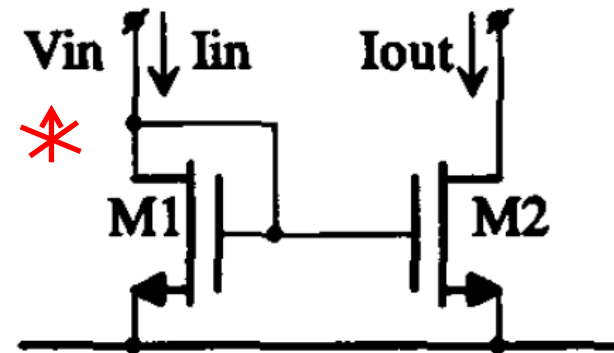The integrated Peak Stretcher: a current mirror used in place of the diode




Peak Stretcher implemented with CMOS

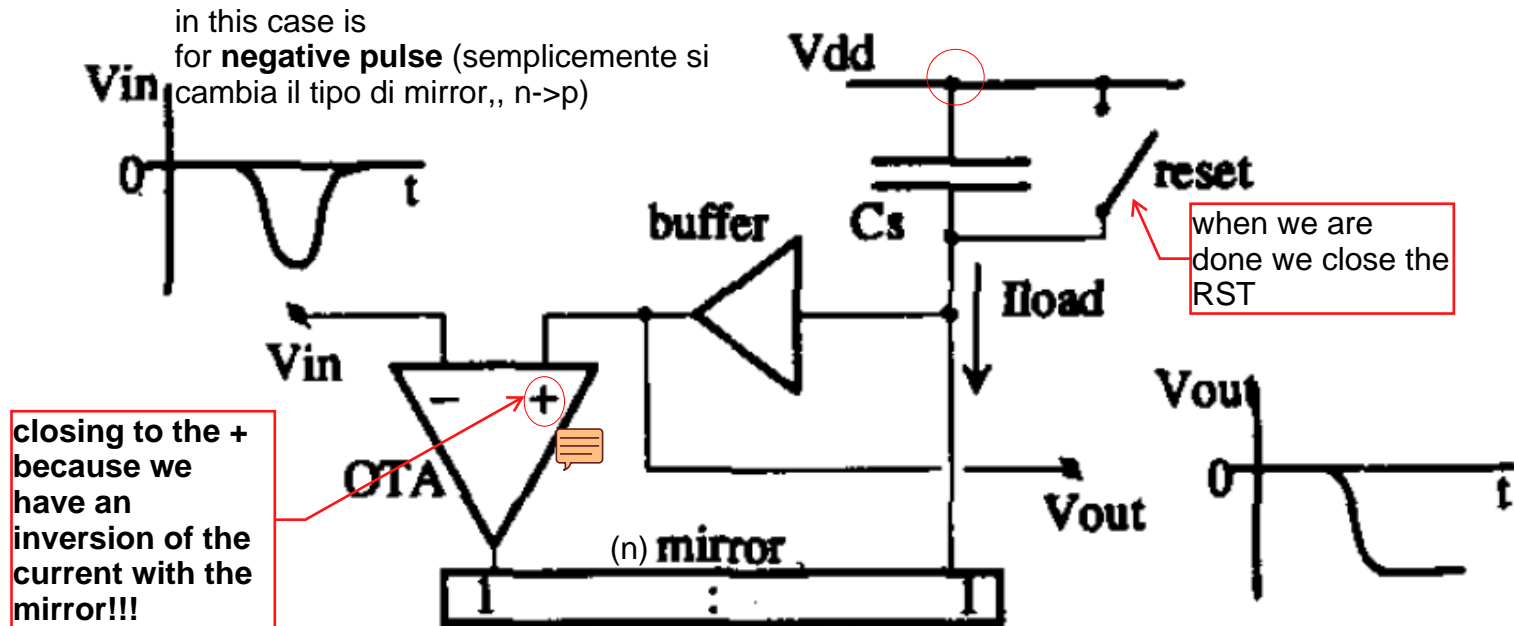

1. input drops down, is lower than V_+ , a current is driven at the output, we are PUSHING a current into the mirror, we have an entering output current in the other part (I_{load}). which is "discharging/dropping" the voltage on VCs. The node drops down, and there's the buffer with a closed loop and tracking of the output. Once we pass the peak the OTA tries to have current in the other direction, but the mirror can't! IT **SWITCHES OFF**! C_s stops to change voltage. We have frozen V_{cs} , and V_+ , and the output voltage.

biasing network for the tail

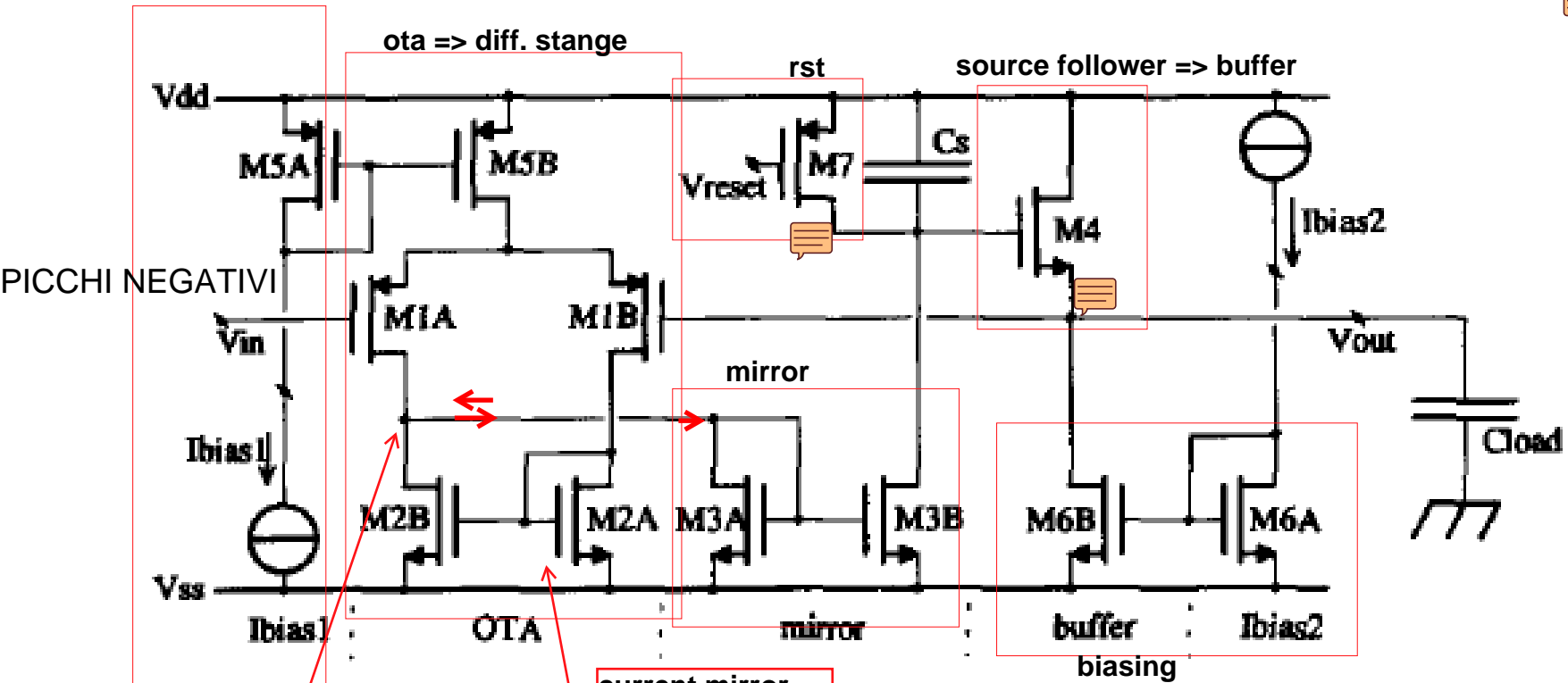


Output of the OTA

$$1) \quad G_{\text{loop}} = -GM_{\text{OTA}} \cdot 1/SC_S$$

$$2) \text{ "Droop rate" } = dV_{out}/dt = (I_{offM7} - I_{offM3B})/C_S$$

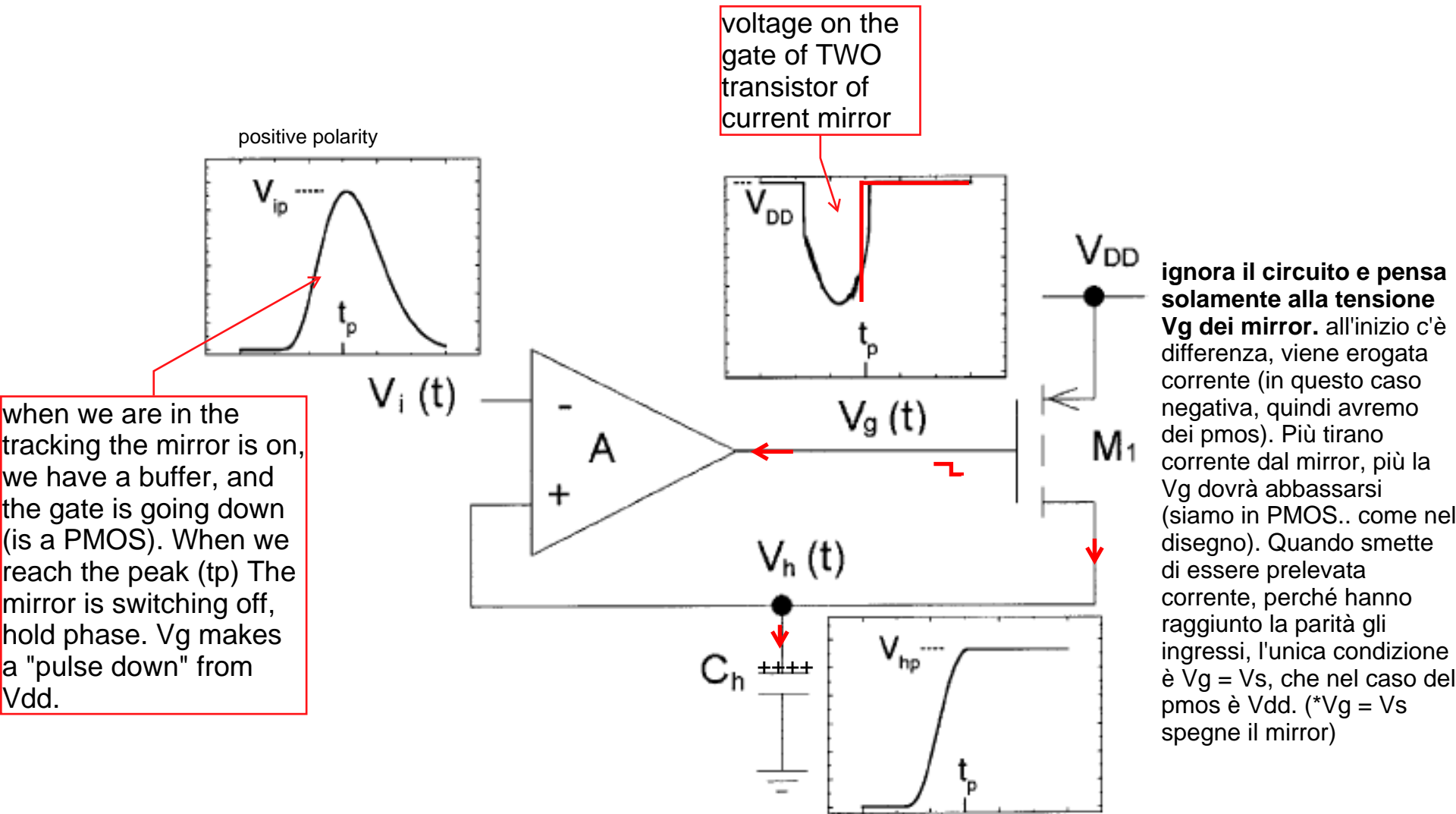3) Figure of Merit? we need to dimension various W/L. \Rightarrow 1. LOOP GAIN (when we are tracking the input, we'd like to have the best possible replica) Cutting the loop at the output and applying a generator, we have the gain, which is the transconductance of the ota (each of the input of transistors), then it feeds into the mirror ($g=1$), then it's converted into V. with Cs ($1/sCs$) then buffer. So we have a frequency dependent loopgain. We need to check the loopgain in the BW of our signal. There's not an unic dimensioning of the loop gain, the design depends on where we have our signal!! if it's high freq. it's hard! if it's at low freq. it's easier. btw this just means: slow gaussian pulses, fast gaussian pulses! [it's more challenging to track the peak of a fast pulse! we have to have a high loopgain] If the loop gain is low, the peak stretch cannot track the steepness of the pulse, and just take a part of amplitude :(We either increase G_{mota} or put a low cap. Indeed if it's small.. it was a good idea to put a buffer!



3 options for the buffer.




Why a buffer: in principle we can do a loop without the buffer and it would work. PROBLEM: it's also the output node. If we close the cap to the output without buffer, it's loaded with external loads. With capacità parassite. Se non facciamo buffer ci vanno in parallelo (come nel CCD)

1. close the loop directly, and then external-to-the-loop buffer. Not usually a good idea, because we introduce the NL of the buffer.


2. BEST! use a "nice buffer", opamp in buffer mode ($V_{out}=V_-$), inside the loop, preserving the quality of output vs input, b/c buffer is in the input. Problems: we introduce in the loop the singularity of buffer TDF. So for stability of loop we need to consider also the pole of the buffer. BTW when the loop is closed the overall circuit is a buffer.. which is usually the most probable to be unstable (lowest gain, largest BW).

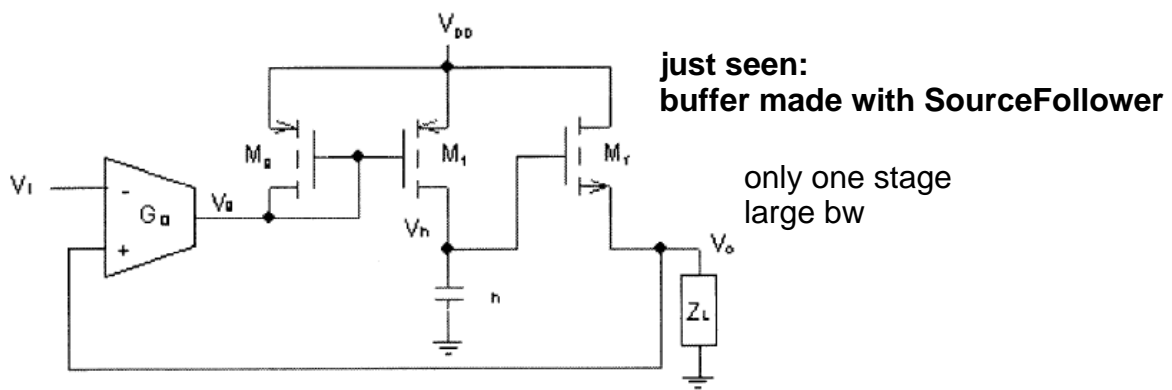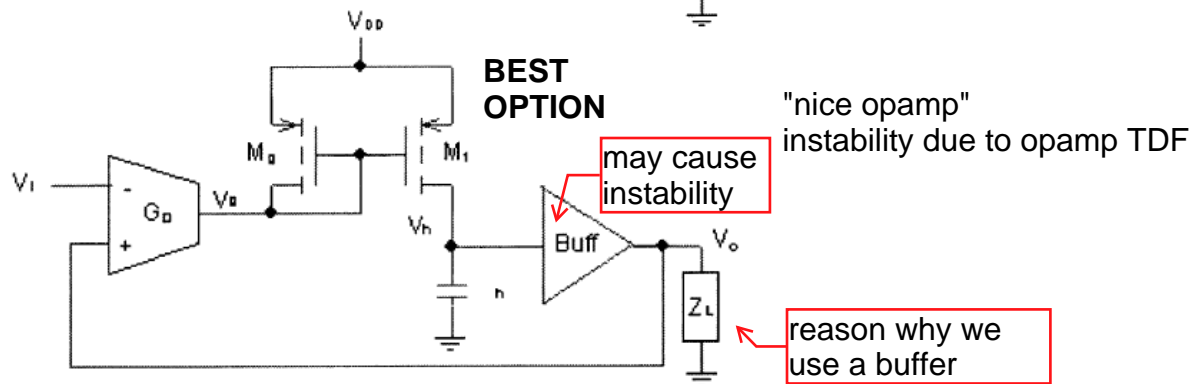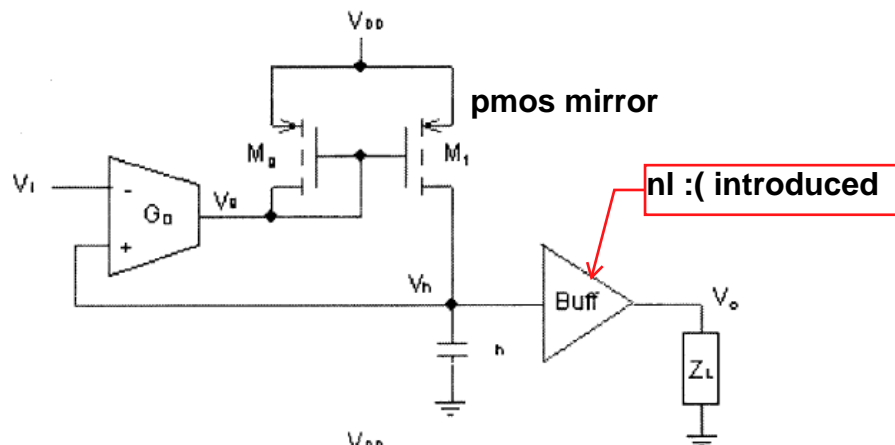3. advantage: just single stage transistor, which usually has a large BW.

same circuit for positive polarity: same circuit just flipped for polarity.



negative pulse

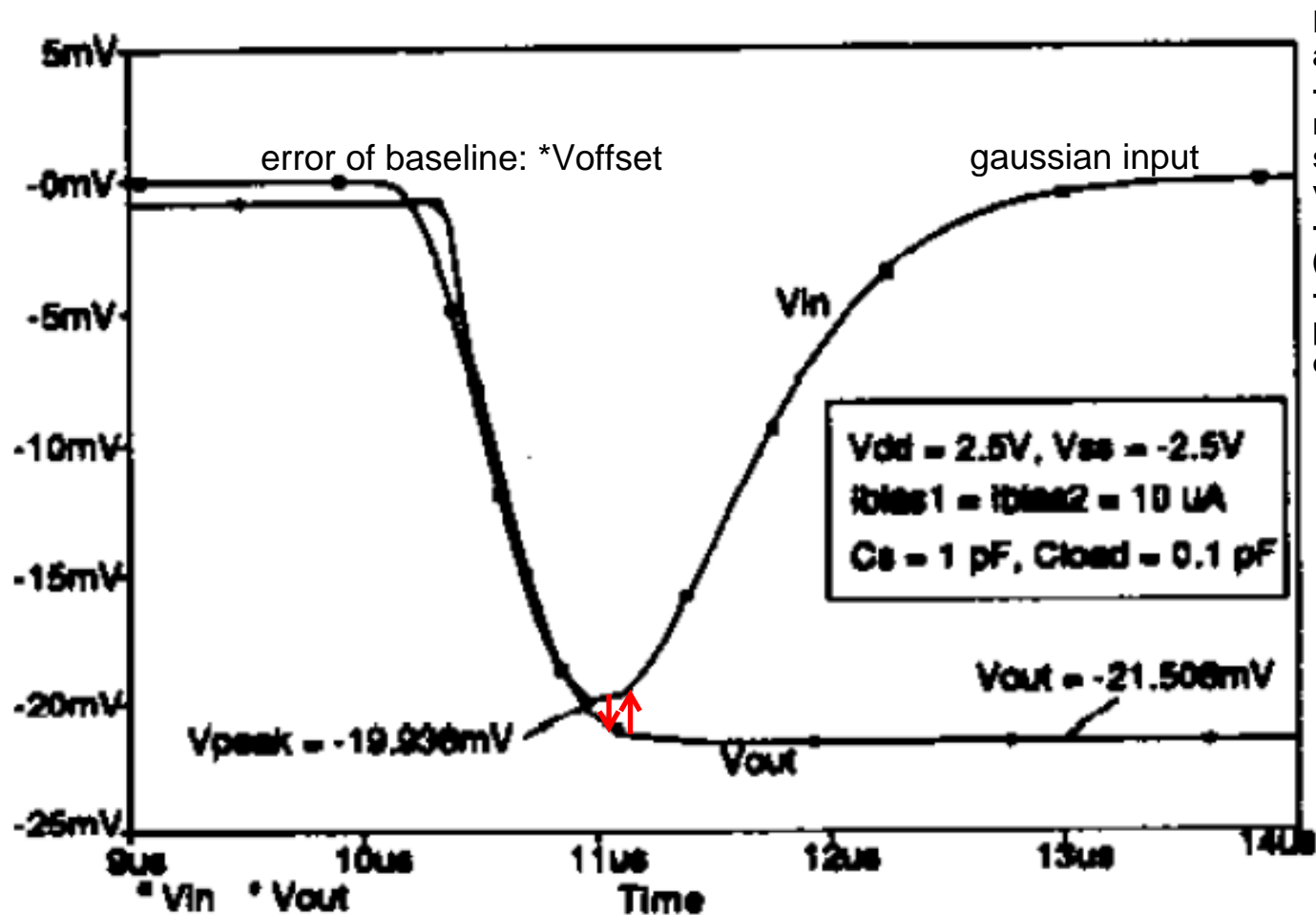


Per il max abbiamo:

- overshoot (il mirror non si è spento abbastanza velocemente)
- undershoot (GLOOP basso)
- overshoot/undershoot presenza di un offset dell'opamp

DC offset and error on V_{out} limited by OTA bandwidth and by the speed of the current mirror to switch off

The gap represent how good/bad you were in the design. If the loop gain is limited we can't track very well. Extra voltage: b/c the mirror has to be switched off,, but if the speed of the loop is not sufficient to turn it off, for a small time we give current to the cap, which is extra charged.

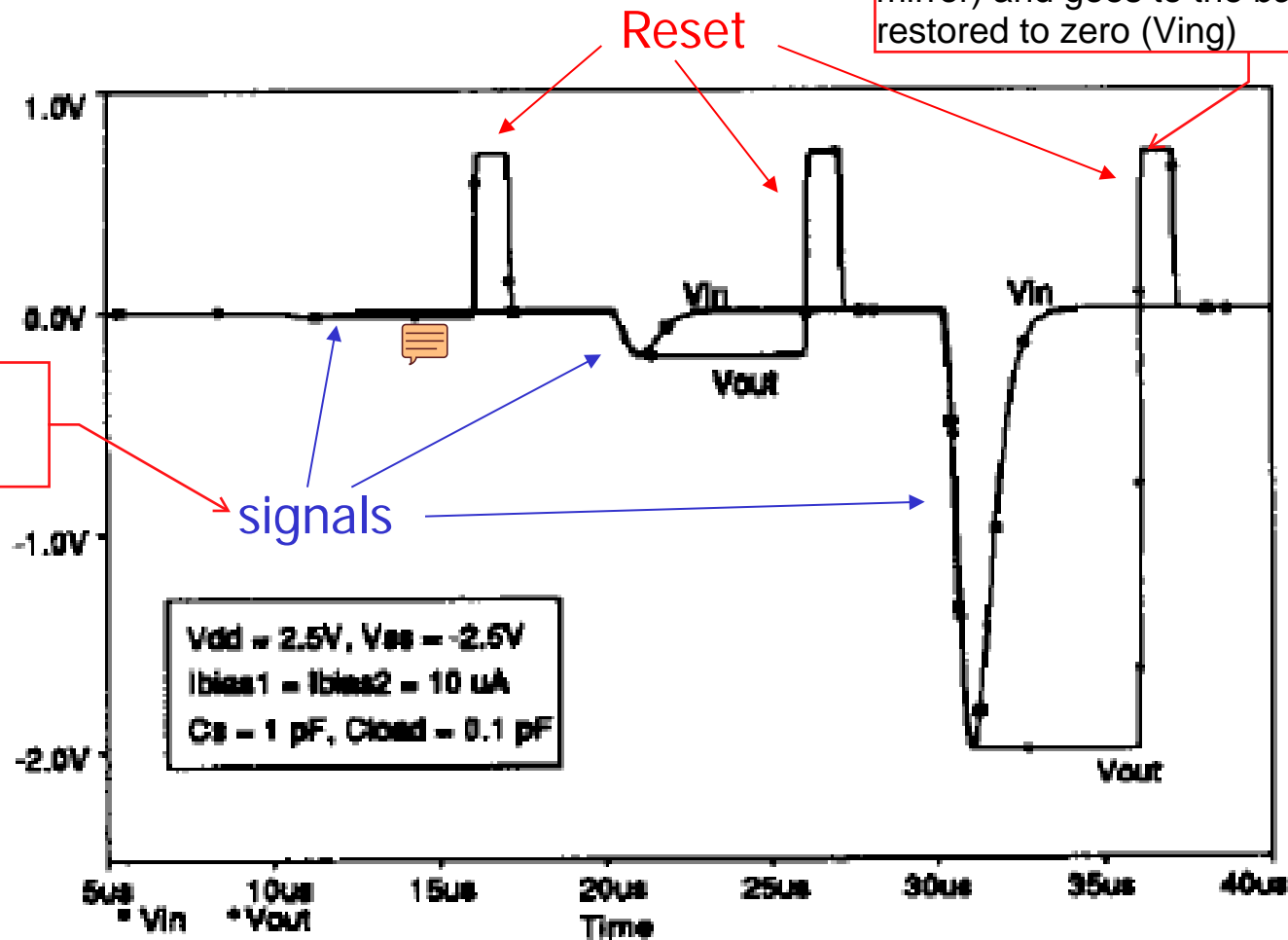
you don't reset to ground but to vdd. Once you release the peak stretcher finds itself in tracking mode! So it turns on (the current mirror) and goes to the baseline, while it's restored to zero (V_{in})



Why resetting to V_{dd} : this way we can automatically track the baseline of the shaper, whatever it is. (Zero in the graph... won't really be zero). In questo modo possiamo fare il tracking verso ogni baseline.. se il cap. fosse stato chiuso vs ground non possiamo essere certi che fosse uguale al ground di ingresso. Whatever pulse we have, same reset. (*Ma cmq) if the loop is not perfect, again the tracking of baseline is not perfect (slide 7). significa semplicemente che se c'è voffset allora nemmeno il tracking della baseline viene fatto correttamente!

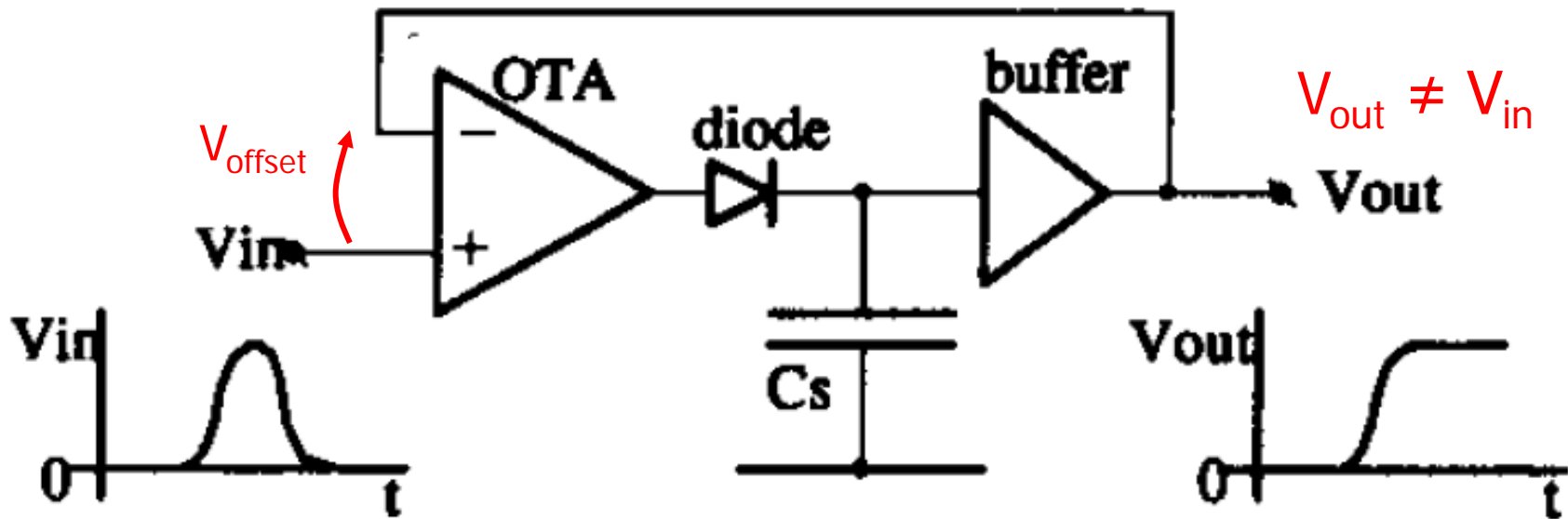problem: OFFSET OF THE OTA, due to mismatch of differential pair. Oddp => not 0 output => means Voffs at the input. Simply means, output not equal to the input, $V_{out} = V_{in} + V_{offs}$.


Limit of the traditional configuration (with both diode and mirror configurations): offset of the OTA




This is a problem if we want output exactly equal to the input. SOLUTION: next slide

Solution: "two phases" peak stretcher

traditional peak stretch, tracking phase

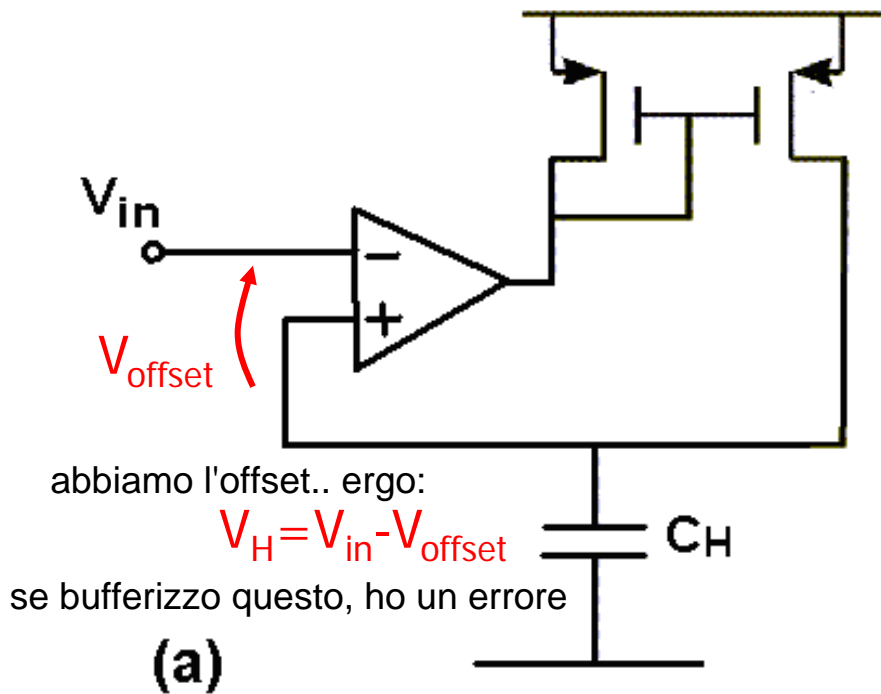


a) normal operation

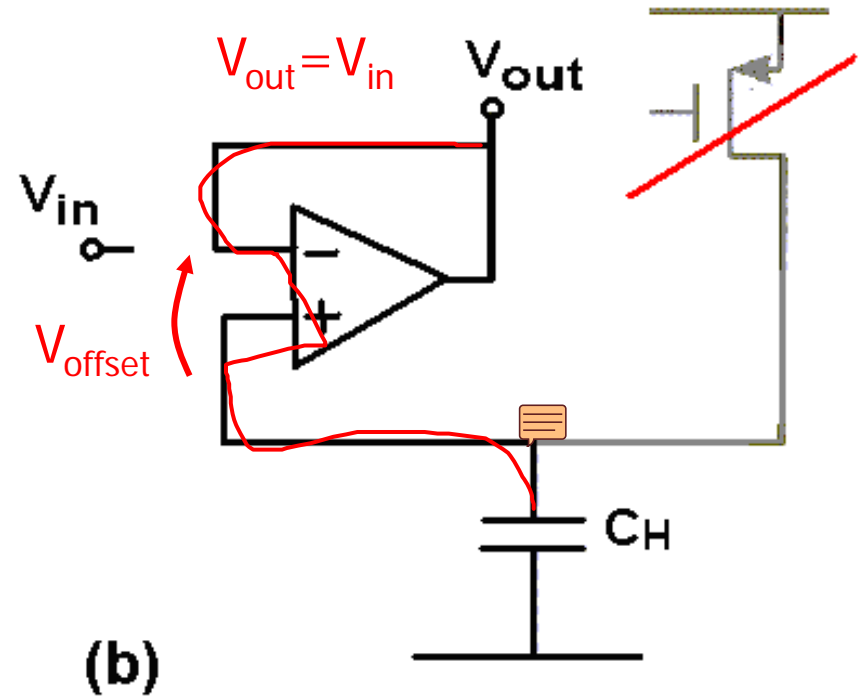

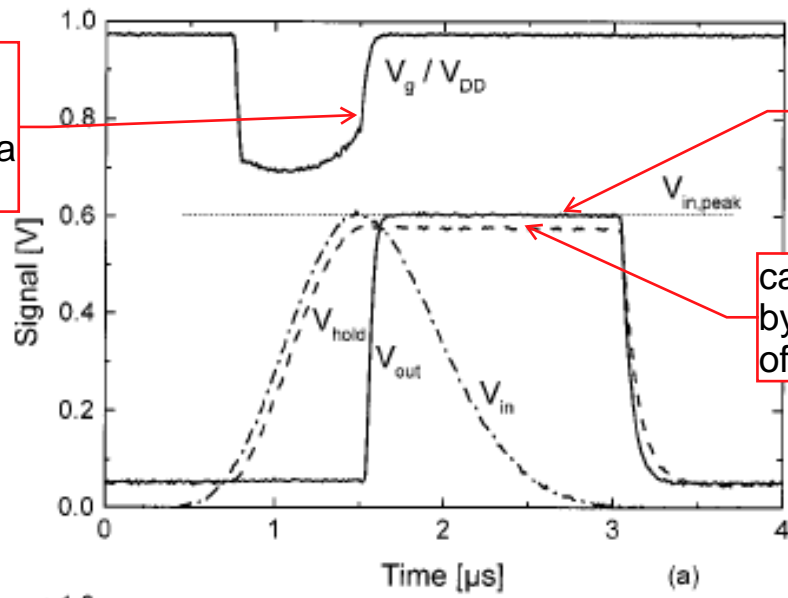b) amplifier operated as buffer


il vgate
sparisce
quando inizia la
fase di hold!!



voltage amp. closed
as a buffer. THE
OUTPUT IS
IDENTICAL!

case: affected
by negative
offset.

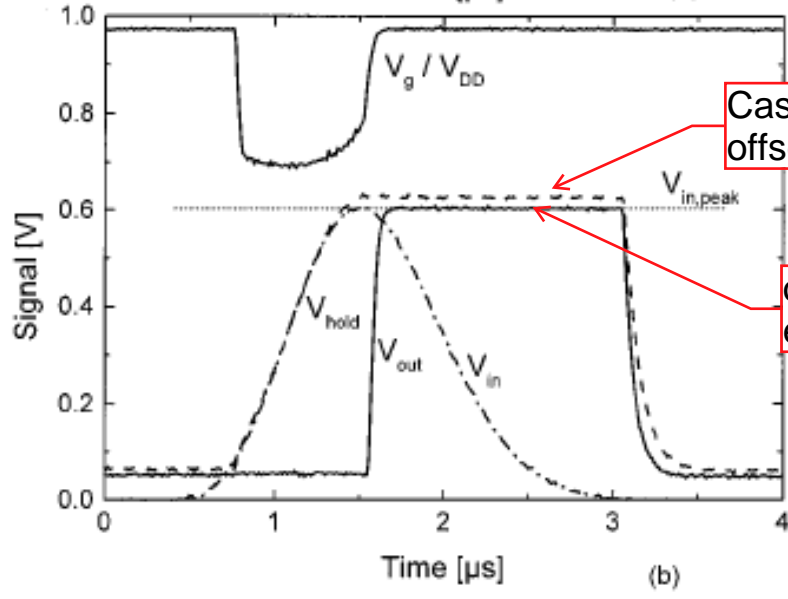example of response in
case of offsets with
opposite sign



Case: positive
offset


output of buffer
equal!

(V_g : gate voltage of the
mirror MOSFETs)



Con gli switch di cui ho bisogno....

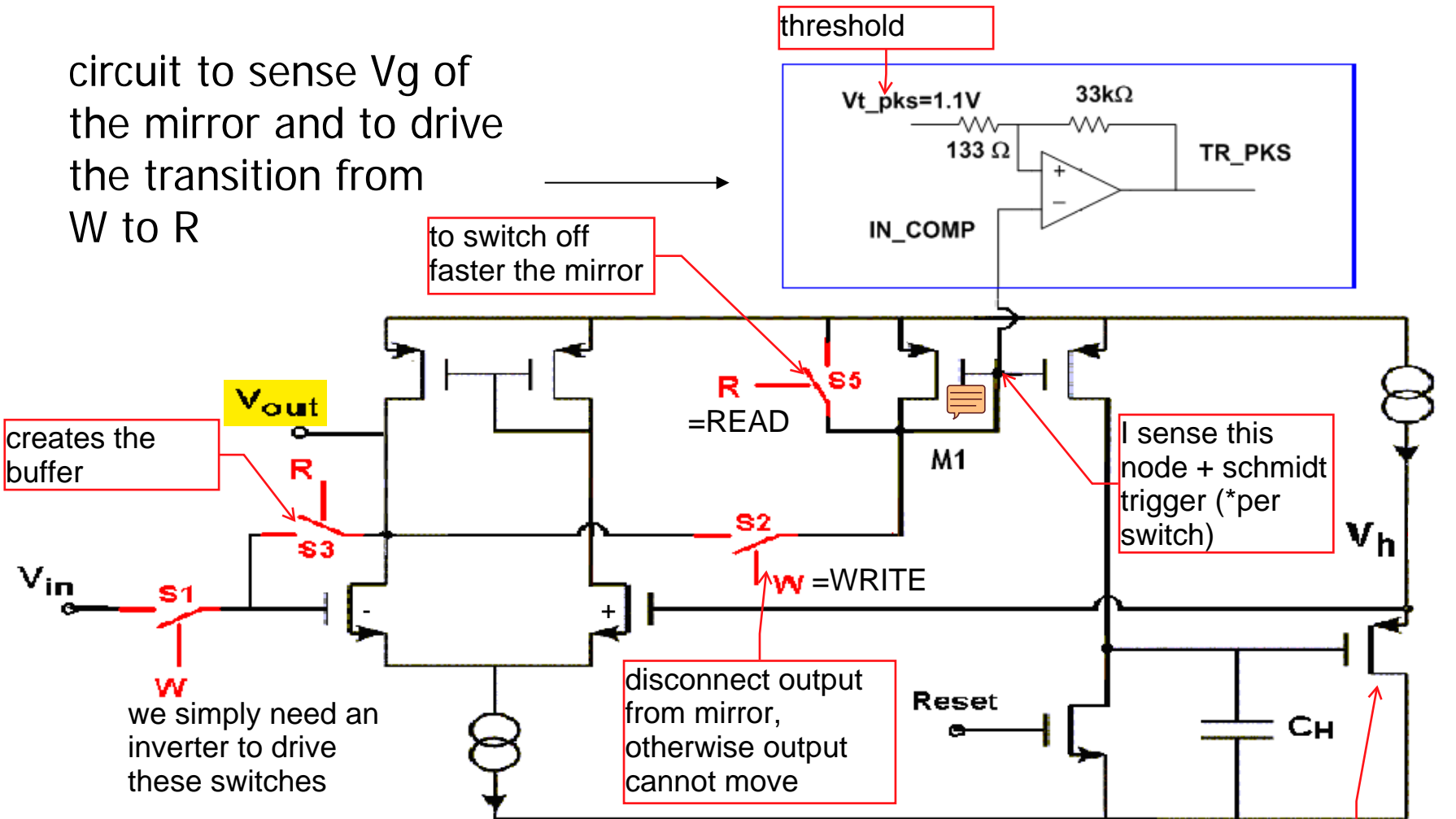circuit to sense V_g of the mirror and to drive the transition from W to R



(*impulsi positivi)

W: write (tracking) R: read (hold)

nota che in questo esempio c'è lo stesso il buffer

Quindi.. che segnale digitale usiamo per fare il driving di questi switches? IL GATE VOLTAGE $V_g(t)$, che fa una sharp transition quando sono al peaking time. Quindi, il trigger per il transformation è generato autonomosly using V_g .

Derandomization of the events


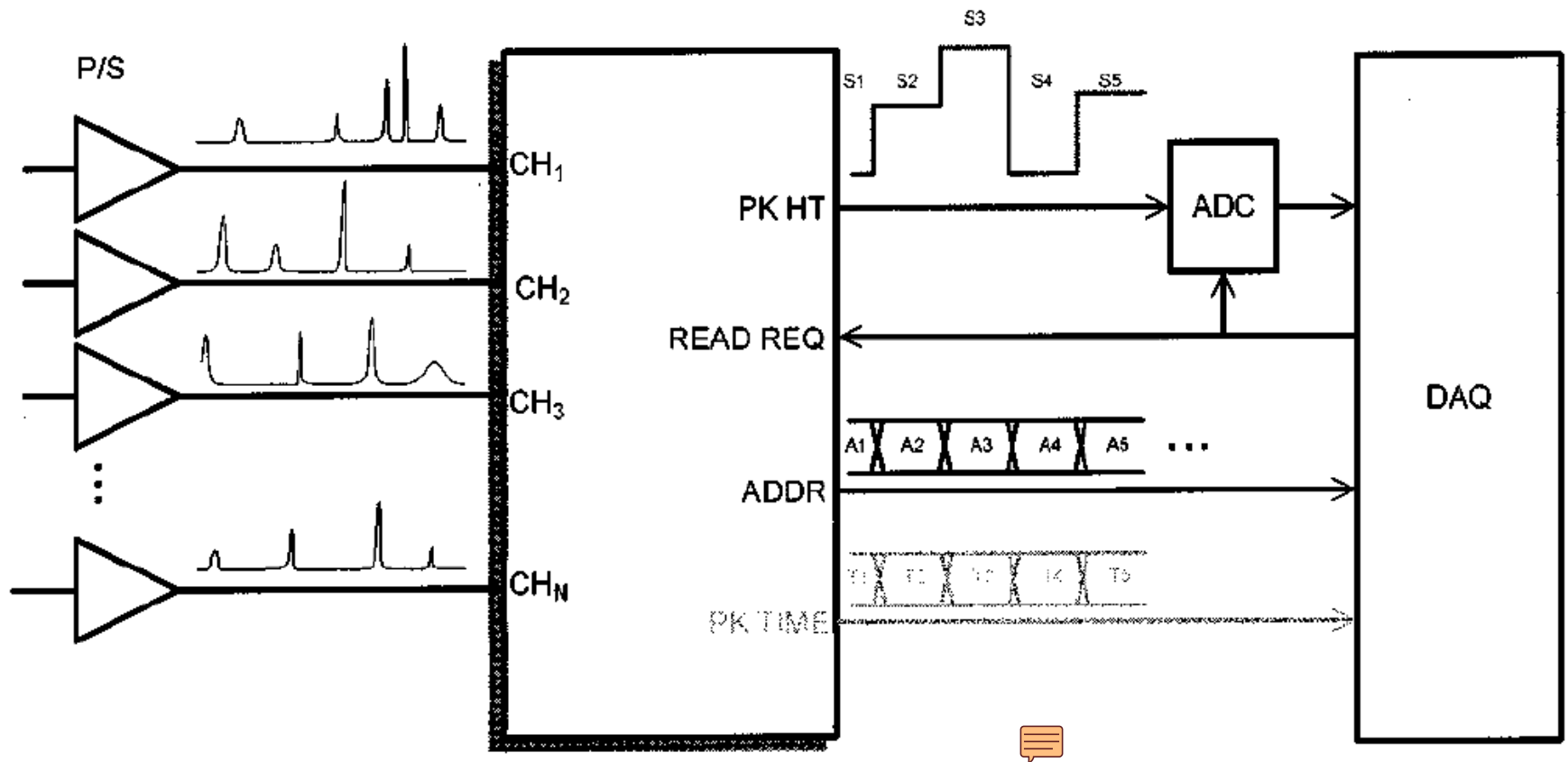



Fig. 6. Ideal self-triggered, self-sparsifying, derandomizing, and dead-timeless multichannel readout system.

Powerful use of peak stretcher: **ANALOGUE MEMORY** (as long as the ADC has not converted, we have a storing of the analogue value of V_{in_peak}). We can use this to solve problem in pulse processing for detectors: photons in the various channels arrives totally random. Vorremmo un adc che va in running con una det. frequenza però : (disegno quaderno. Ovviamente se $t_{adc} = \text{average arriving pulse}$, non è abbastanza, perché significa che abbiamo gruppi di eventi che arrivano più velocemente, ed altri più lentamente.


CASE: SINGLE INPUT, in caso di arrivo viene
connesso al primo peak stretcher available (che quindi non è in attesa di essere letto)

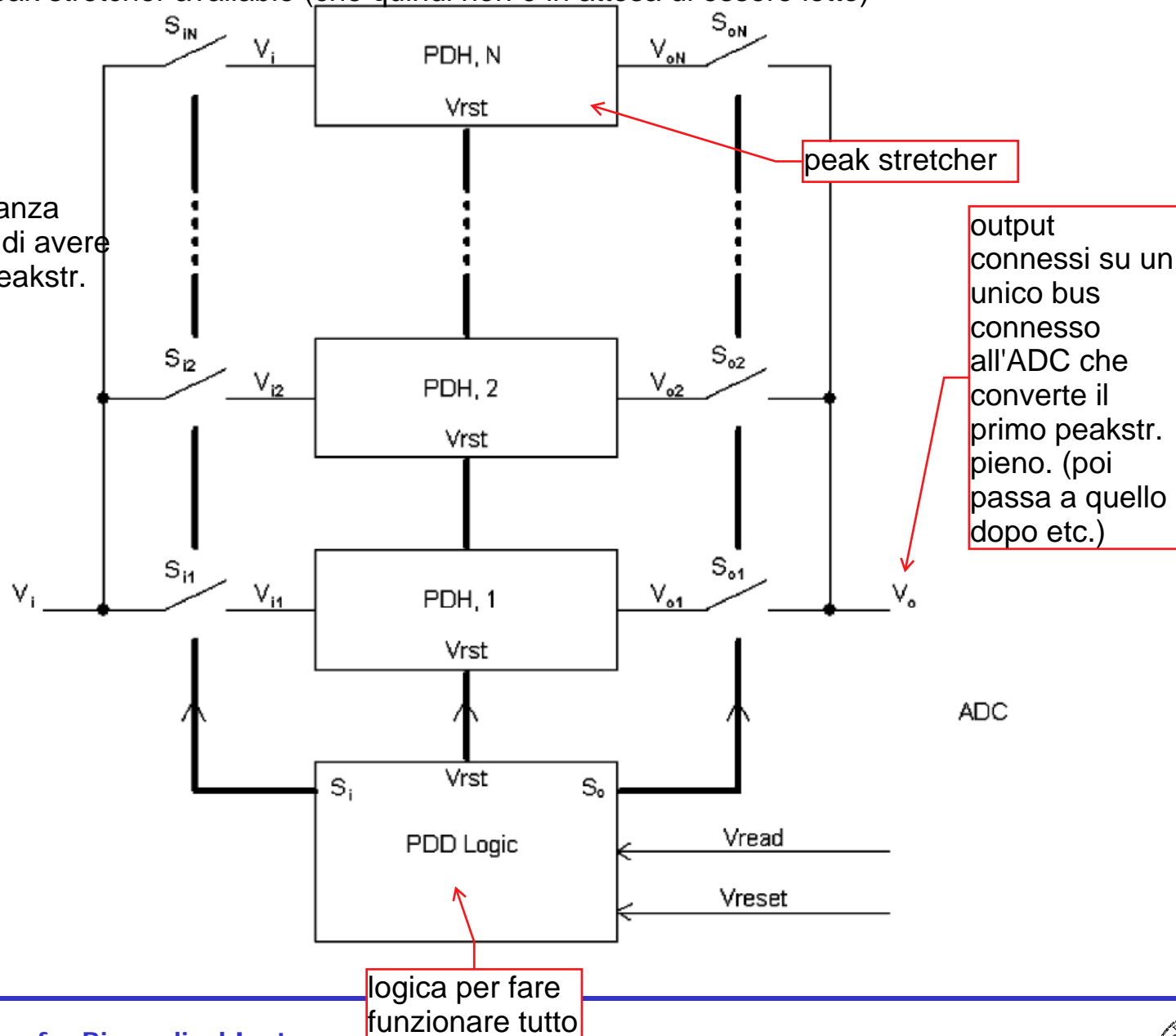Dobbiamo avere N
peakstretcher abbastanza
grande per garantire di avere
sempre almeno un peakstr.
free.



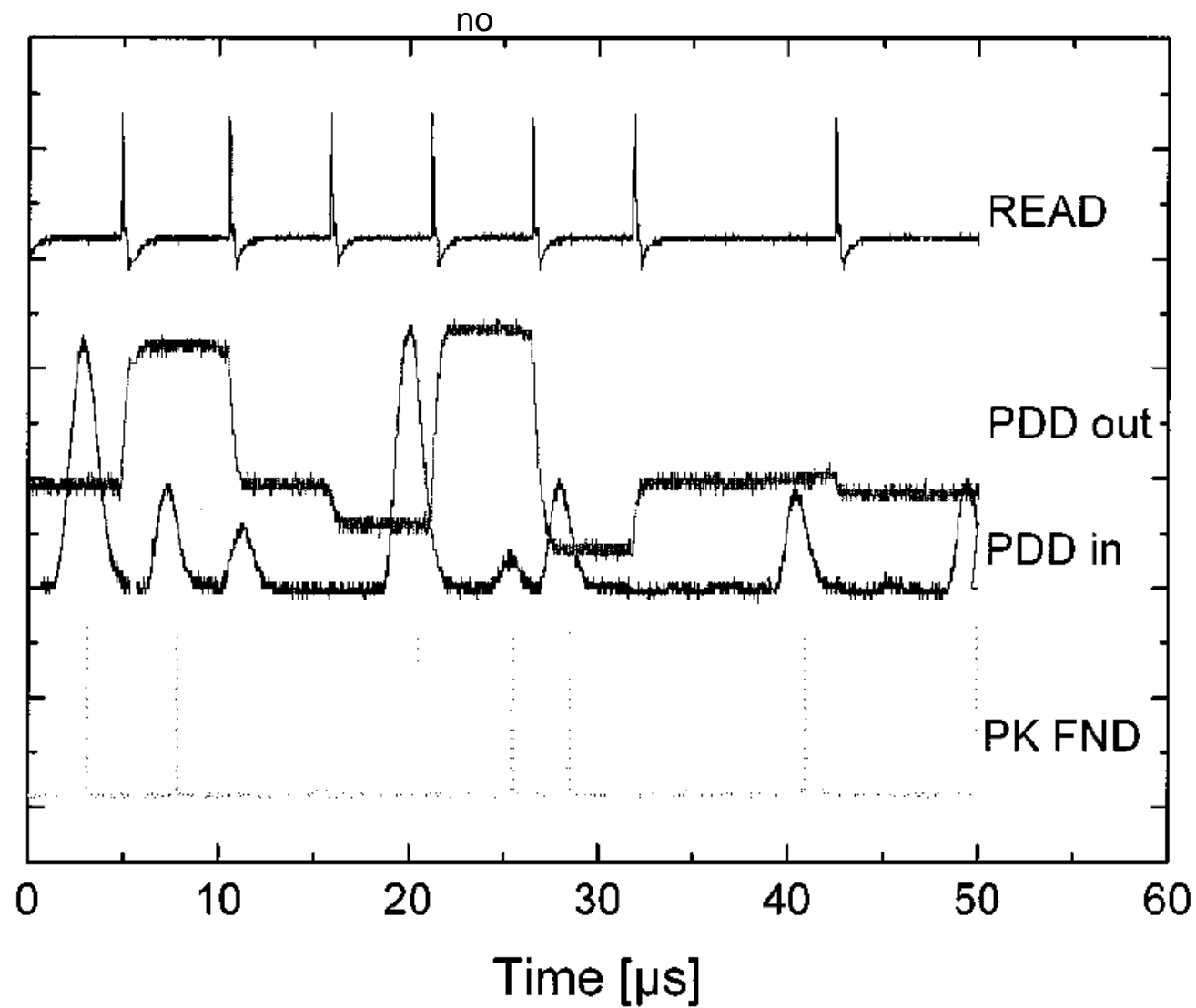

..how it works

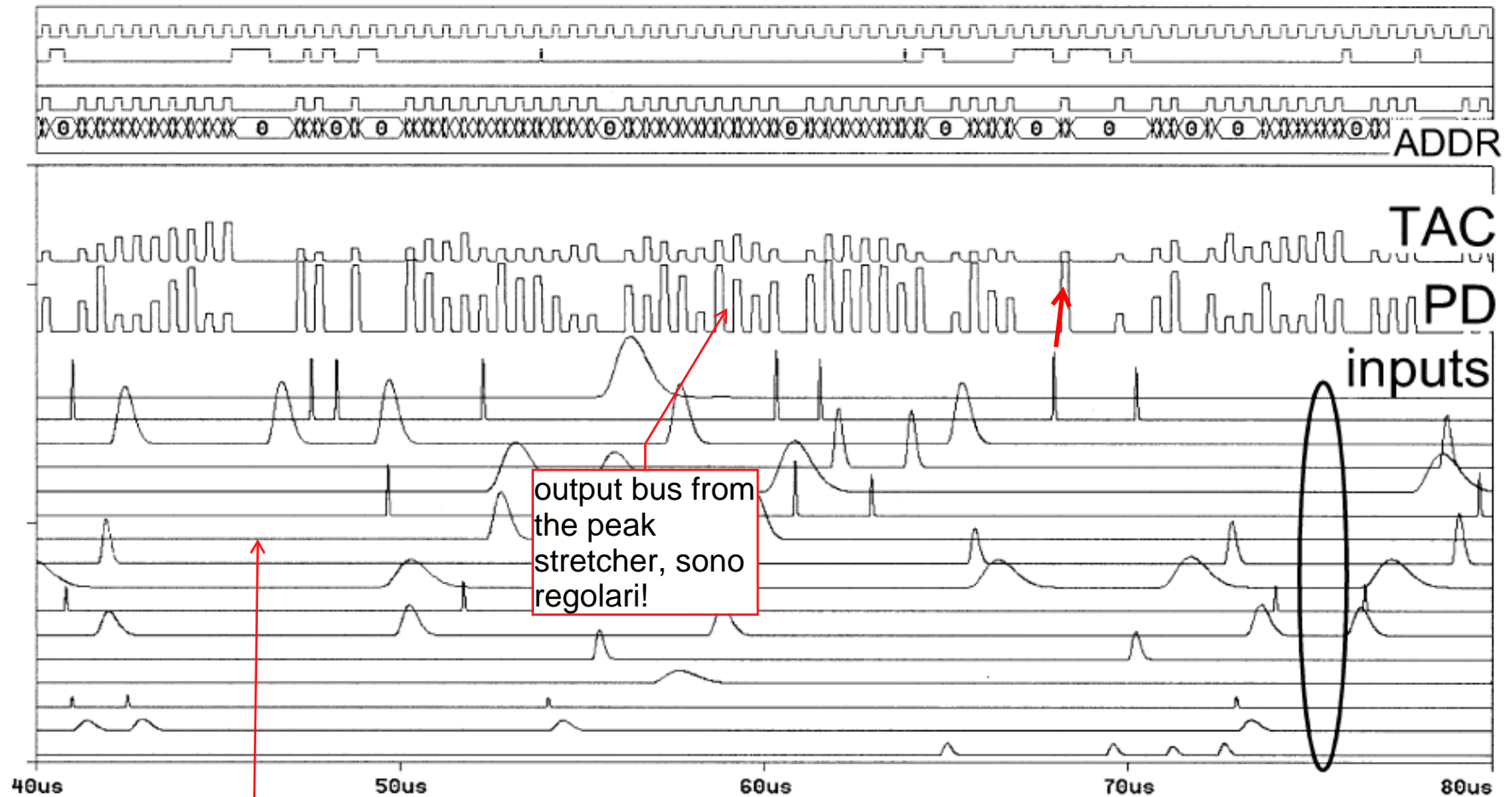

nessuna gaussiana è persa! abbiamo semplicemente un sequencing.

gausiane che
arrivano a caso